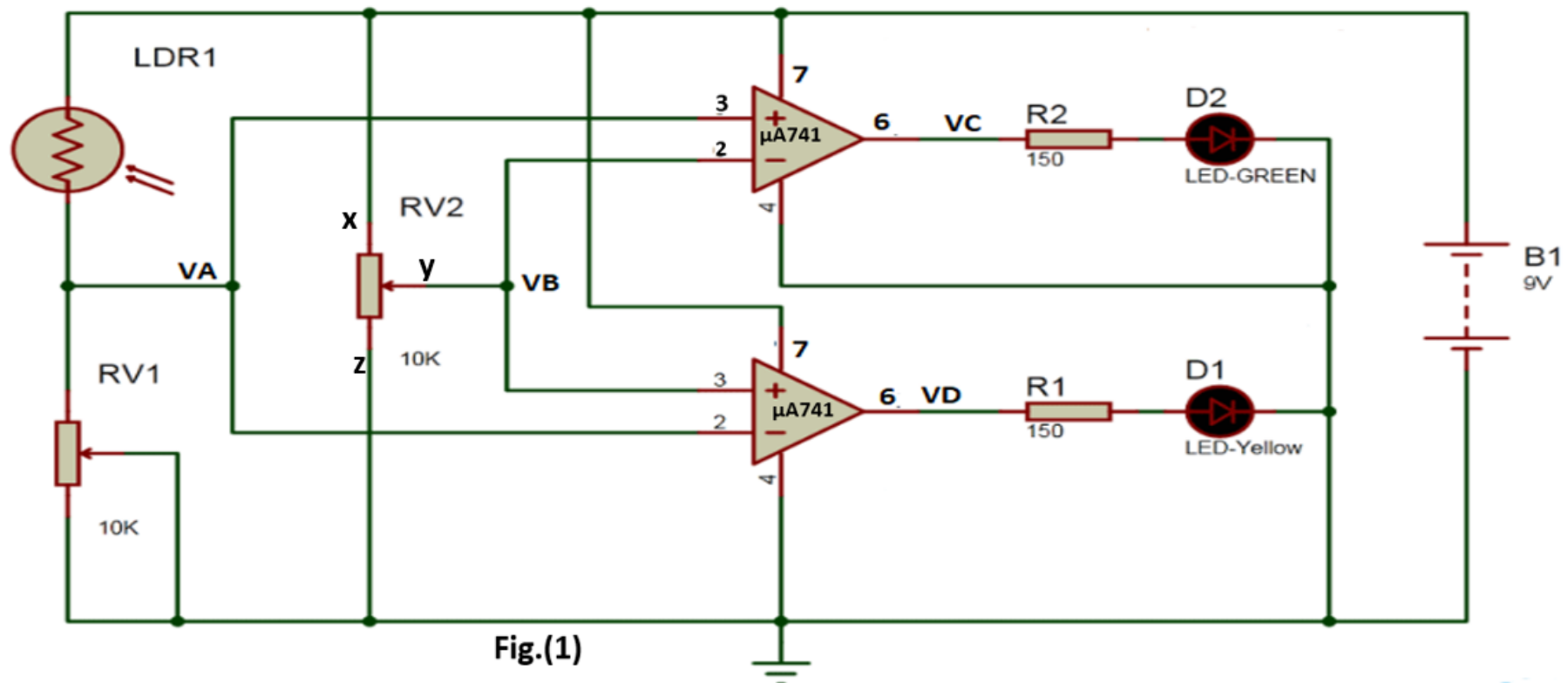


ENEE2360 Project sem1 2024-2025

Dark and light Indicator Circuit

The circuit shown in Fig(1) is used to indicate if there is a dark or light in the surroundings. Some applications of this circuit, are street light controlling, home /office light controlling day and night indicators, etc.



Part 1: Practical Part

- a) Construct the circuit shown in Fig.(1).**
- b) Adjust the resistance of RV1 and RV2 so that D1 will glow only at night and D2 will glow only during the day.**
- c) Measure and record all the nodal voltages at night.**
- d) Measure and record the resistances R_{xy} , R_{yz} , and the LDR sensor at night**
- e) Measure and record all the nodal voltages during the day.**
- f) Measure and record the resistances R_{xy} , R_{yz} , and the LDR during the day**

Part2 :(Simulation and reporting)

- a) Replace the LEDs with D1N4148 diodes.**
- b) Replace the LDR sensor with a variable resistor.**
- c) Adjust RV1 and RV2 to the values obtained in step (b) of the practical part**
- d) Simulate the circuit of Fig.(1) for $R_{\text{sensor}} = 100\Omega$ and determine all the nodal voltages and the diodes' status.**
- e) Repeat step (d) for $R_{\text{sensor}} = 200\Omega, 500\Omega, 1K\Omega, 10K\Omega, 50K\Omega, 100K\Omega$ and $500K\Omega$.**
- f) Write a simple report which includes:**
 - 1 – Explanation of the function of the circuit of Fig.(1)**
 - 2 - Simulation circuits and results**
 - 3 - Comparison of simulation results to hand calculation**
 - 4 – Conclusion**